

Christopher Hunt

Homework Assignment #2

ENGR 201

2.1

An electric car charges at a rate of 12.0 kW for exactly 5 hours and is then able to travel 256.4 miles on that charge. If electricity costs \$0.115 per kWh, what is the cost the electrical 'fuel' to drive the car in dollars per mile driven?

Variables:

$$p = 12kW \quad t = 5hr \quad price = \$0.115 \quad d = 256.4mi \quad cost = p * t * price$$

Calculations:

$$cost = 12kW * 5hr * \$0.115 \Rightarrow cost = \$6.90$$


$$\frac{cost}{mile} = \frac{cost}{d} = \frac{\$6.90}{256.4mi} \Rightarrow \frac{cost}{mile} = \$0.026$$

Solution:

$$\frac{cost}{mile} = \$0.026$$

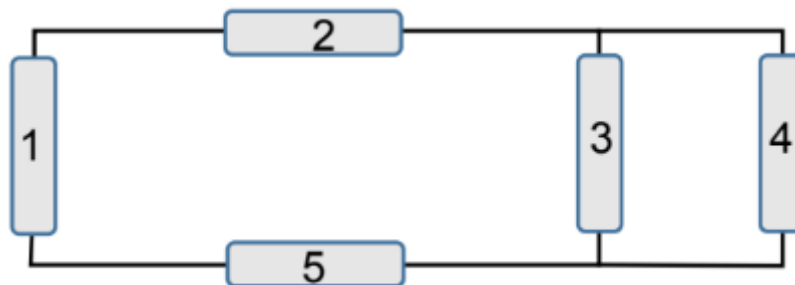2.2

In the diagram below there are 5 circuit elements. If $P_1 = -50\text{ W}$, $P_2 = 35\text{ W}$, $P_3 = -15\text{ W}$, and $P_4 = 50\text{ W}$, what is the power, P_5 in watts?



Variables:

$$P_1 = -50W \quad P_2 = 35W \quad P_3 = -15W \quad P_4 = 50W \quad P_5 = ?$$

Calculations:

P_5 can be found using the Law of Conservation of Energy $\Rightarrow \sum p = 0$

$$-50W + 35W - 15W + 50W + P_5 = 0 \Rightarrow P_5 = -20W$$

Solution:

$$P_5 = -20W$$


2.3

Find V_o in the circuit shown below.

To solve we must use Kirchhoff's Voltage Law, which states: The sum of all the voltages around a loop is zero at every instant

$$\sum v_{loop} = 0 \equiv \sum v_{rises} = \sum v_{drops} \text{ around the loop}$$

We will use the loop indicated below:

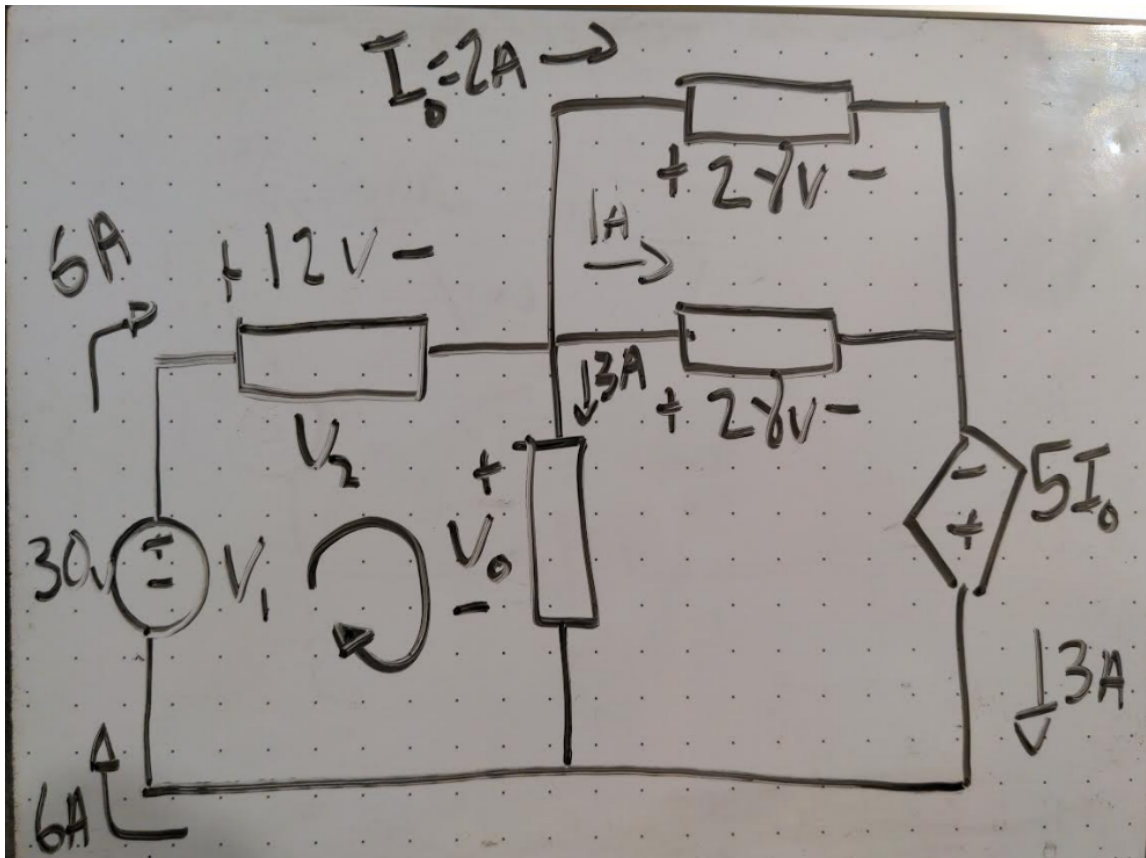

Variables:

$$v_o = ? \quad v_1 = 30V \quad v_2 = 12V$$

Calculations:

$$-30V + 12V + v_o = 0 \Rightarrow v_o = 18V$$

Solution:

$$v_o = 18V$$

2.4

The resistivity (ρ) of carbon is $4.0 \times 10^{-5} \Omega \cdot m$. What length of 2.0 mm diameter carbon rod would be required to make a 1.0Ω resistor?

Variables:

$$\rho = 4.0 \times 10^{-5} \Omega \cdot m \quad d = 2.0 \text{ mm} = .002 \text{ m} \quad r = \frac{d}{2} = .001 \text{ m} \quad R = 1.0 \Omega \quad l = ?$$

Calculations:

We will use the formula $R = \rho * \frac{l}{A}$ Solve for $l \Rightarrow l = A * \frac{R}{\rho}$:

$$l = (\pi * .001^2) * \frac{1}{4.0 \times 10^{-5}} \Rightarrow l = 0.0785 \text{ m} = 78.5 \text{ mm}$$


Solution:

$$l = 78.5 \text{ mm}$$

2.5

Make a sketch of the following circuit and determine:

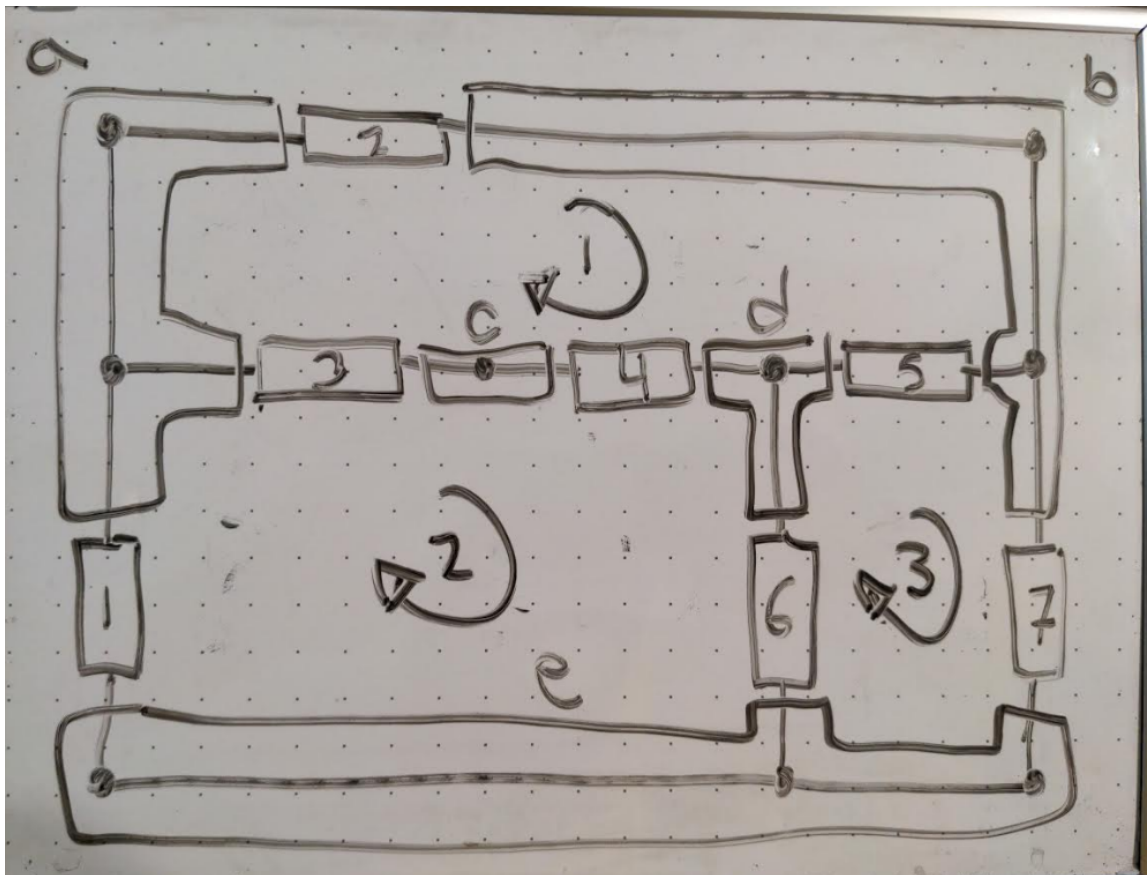- a) the number of branches in the circuit
- b) the number of nodes in the circuit (label the nodes in your sketch)
- c) The number of independent loops in the circuit (show the loops in your sketch)



Solution:

a) Number of branches = 7


b) Number of nodes = 4

c) Number of independent loops = $b - n + 1 \Rightarrow 7 - 4 + 1 \Rightarrow 4$

2.6

The following circuit contains six unknown currents, I_1 through I_6 and critical nodes labeled a through e.

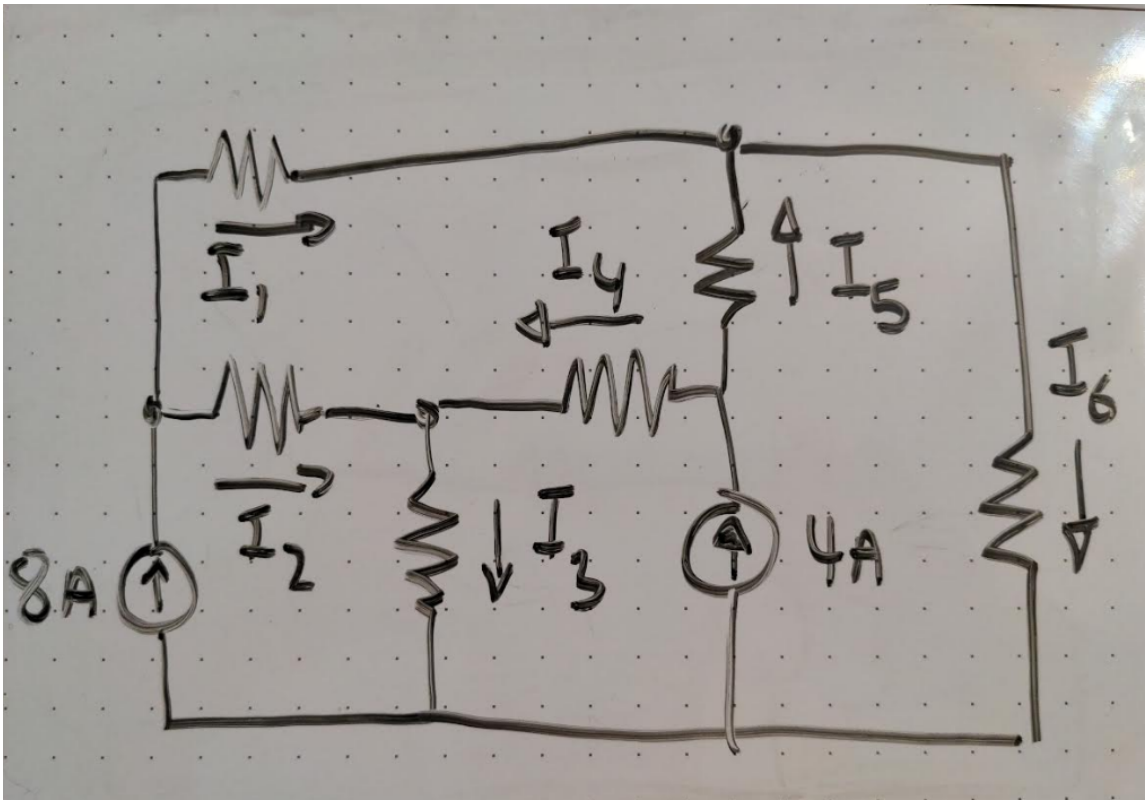a) Write the KCL expression in terms of the currents for nodes a, b, c, and d. b) At this point is there enough information to solve for the currents in the circuit? Explain. c) If $I_2 = 2\text{ A}$ and $I_4 = 3\text{ A}$ what are currents I_1, I_3, I_5 , and I_6 in amperes?



Solutions:

Kirchhoff's Current Law: The sum of the currents entering a node is zero at every instant

$$\sum i = 0 \text{ for every node in a circuit}$$

a)

$$\text{Node A} \Rightarrow 0 = 8A - I_1 - I_2$$

$$\text{Node B} \Rightarrow 0 = I_2 + I_4 - I_3$$

$$\text{Node C} \Rightarrow 0 = 4A - I_4 - I_5$$

$$\text{Node D} \Rightarrow 0 = I_1 + I_5 - I_6$$

$$\text{Node E} \Rightarrow 0 = I_3 + I_6 - 4A - 8A$$

b) There is not enough information to solve because each equation has two or more unknown variables

c) Plug in $I_2 = 2A$ and $I_4 = 3A$ into the equations and solve

$$\text{Node A} \Rightarrow I_1 + 2A = 8A \Rightarrow I_1 = 6A$$


$$\text{Node B} \Rightarrow I_3 = 2A + 3A \Rightarrow I_3 = 5A$$

$$\text{Node E} \Rightarrow I_6 = 4A + 8A - 5A \Rightarrow I_6 = 7A$$

$$\text{Node D} \Rightarrow I_5 = 7A - 6A \Rightarrow I_5 = 1A$$

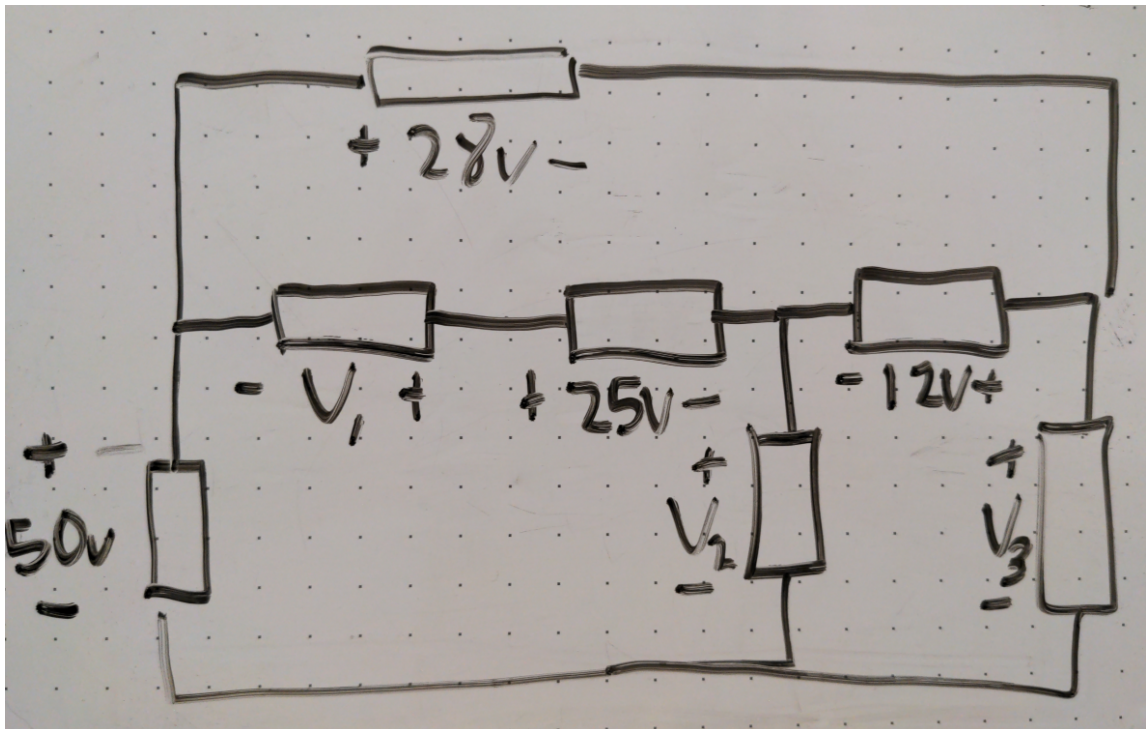2.7

Use Kirchhoff's Laws to determine V_1 , V_2 , and V_3 in the circuit below.



Solutions:

Find v_3 :

$$0 = -50V + 28V + v_3 \quad \text{solve for } v_3 \Rightarrow v_3 = 50 - 28 \Rightarrow v_3 = 22V$$

Find v_2 :


$$0 = -12V + 22V - v_2 \quad \text{solve for } v_2 \Rightarrow v_2 = 10V$$

Find v_1 :

$$0 = -50V - v_1 + 25V + 10V \quad \text{solve for } v_1 \Rightarrow v_1 = -15V$$

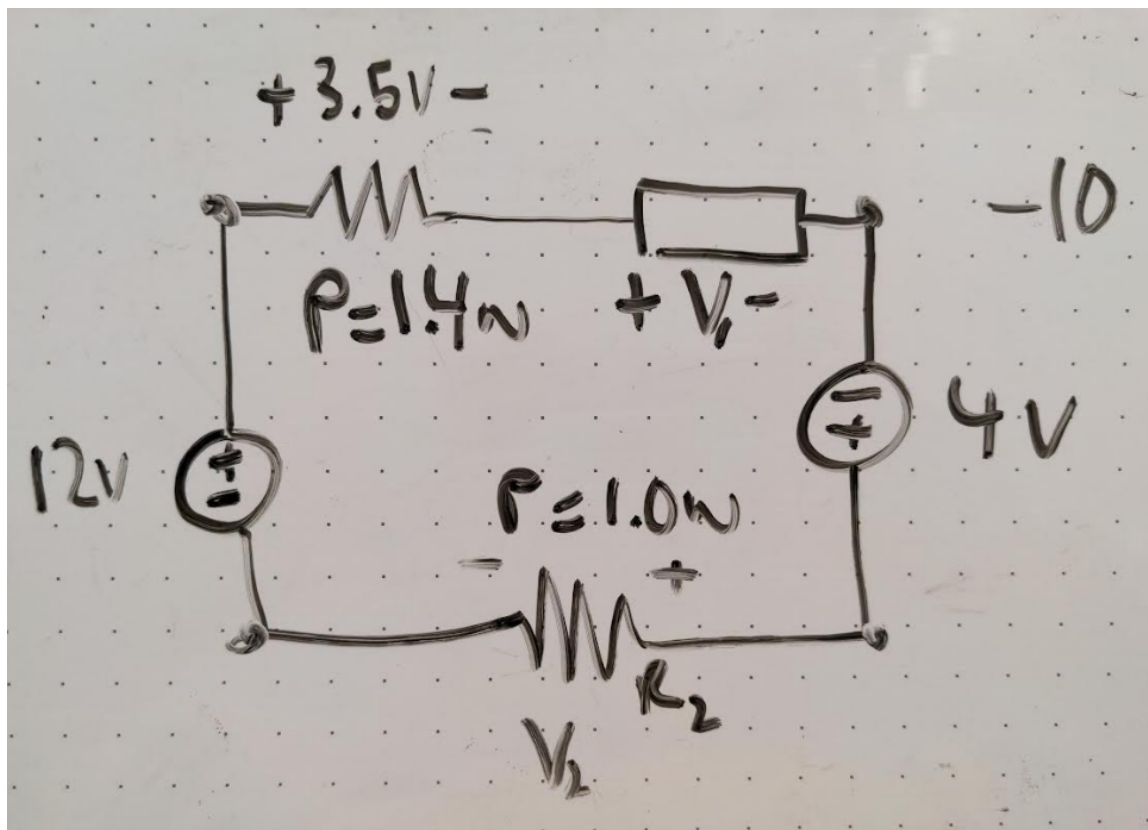2.8

Use KVL and power relationships to determine V_1 in the circuit below:



Solution:

1. Find the current in the circuit using $i = p/v$

$$i = \frac{1.4W}{2.5V} \Rightarrow i = .4A$$

2. Find the voltage across v_2 using $v = \frac{p}{i}$

$$v_2 = \frac{1.0W}{.4A} \Rightarrow v_2 = 2.5V$$

3. Find v_1 using KVL

$$0 = -12V + 3.5V + v_1 - 4V + 2.5V \Rightarrow \text{solve for } v_1 \Rightarrow v_1 = 10V$$