
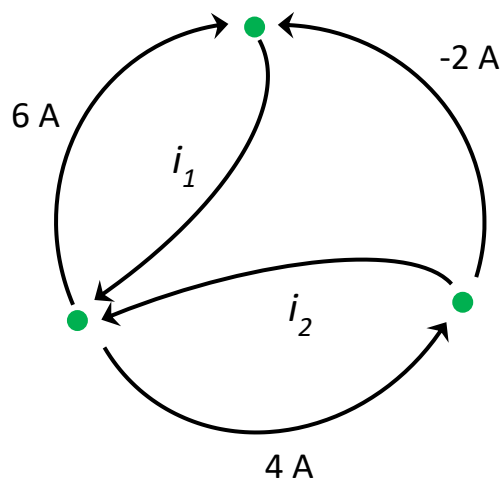


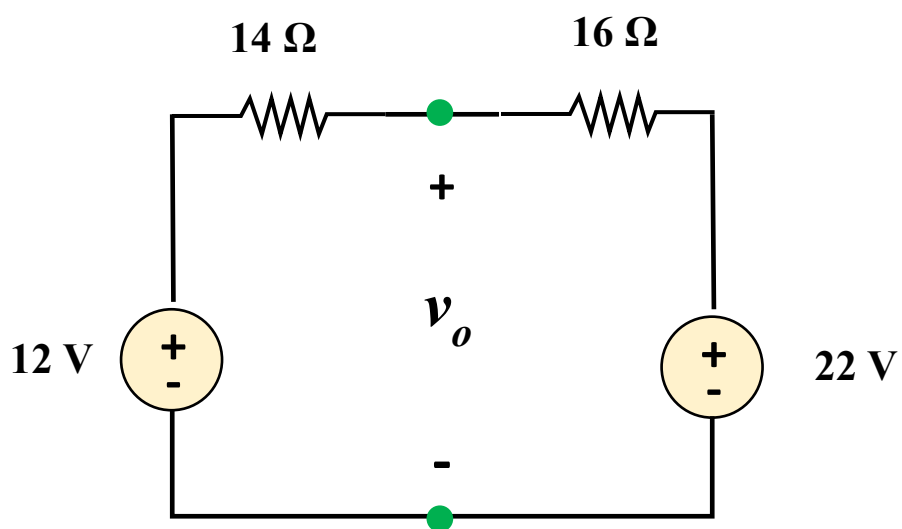
3.1 Determine i_1 and i_2 in the circuit.




3.2 Determine v_o in the circuit below




3.3 Calculate v and i_x in the circuit.

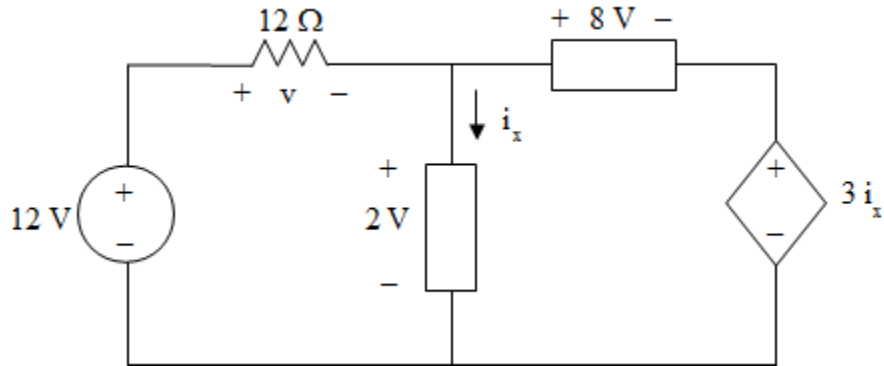


3.4 Find V_x in the circuit.

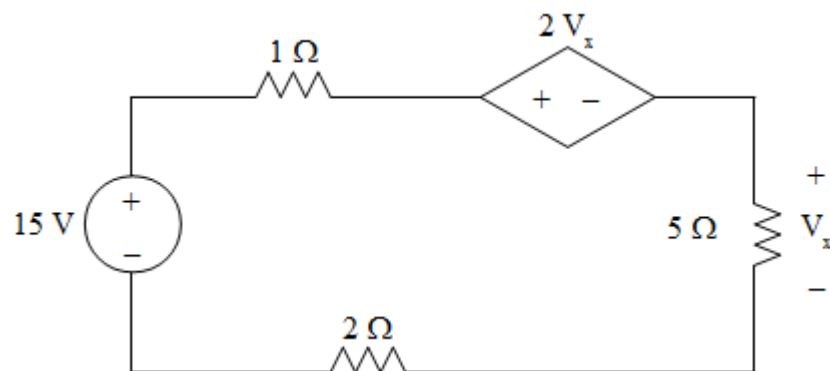

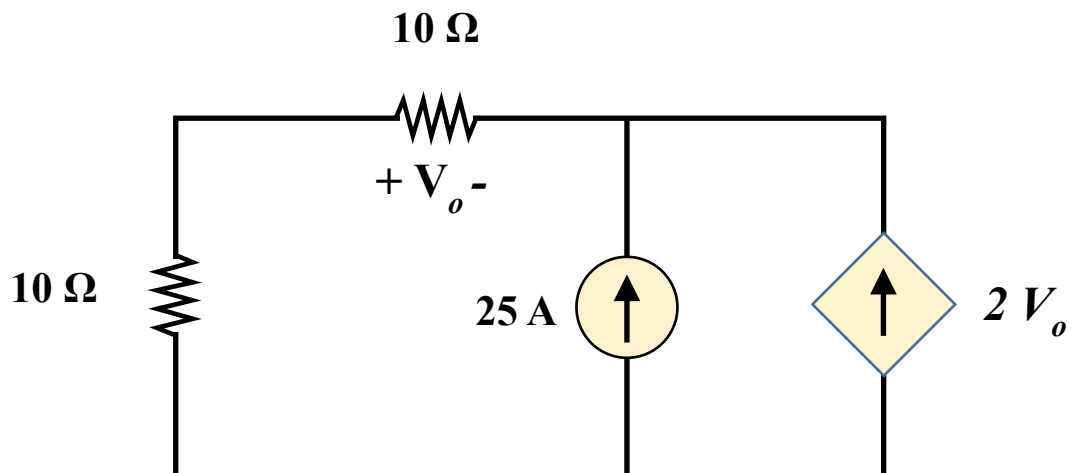
3.5 Find the voltage, V_o in the circuit below and calculate the power absorbed by the dependent source.



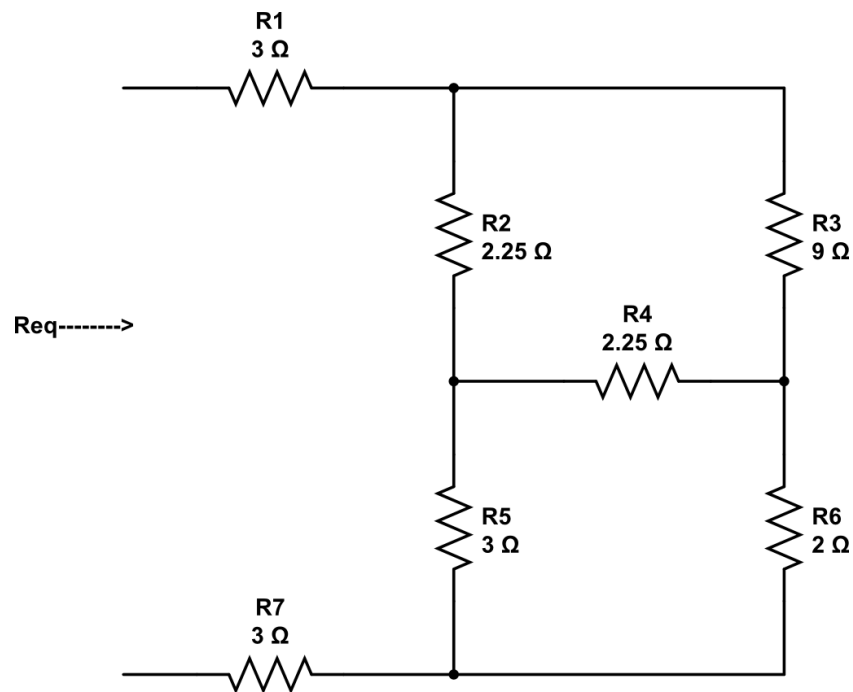3.6 Use the wye-delta transformation to find R_{eq} , for the circuit below



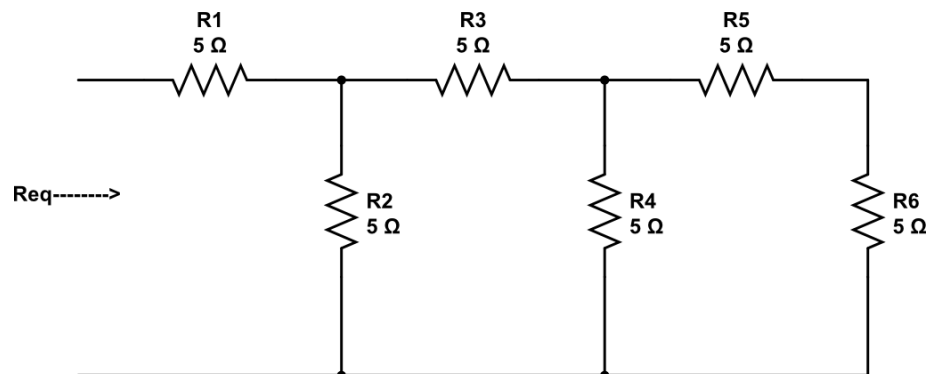3.7 Determine R_{eq} for the circuit below



3.8 Using series/parallel combinations find the equivalent resistance seen by the source in the following circuit.

